
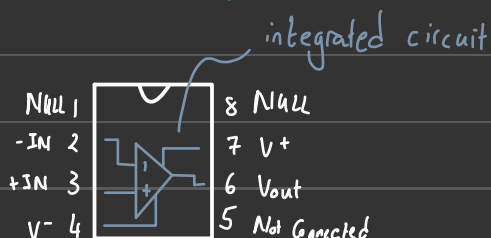



Operational Amplifiers:

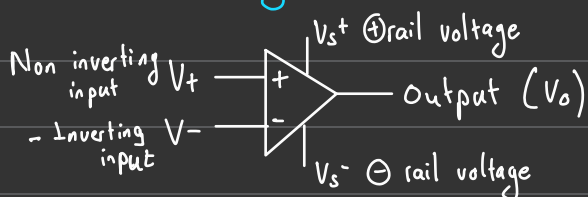


Symbol:



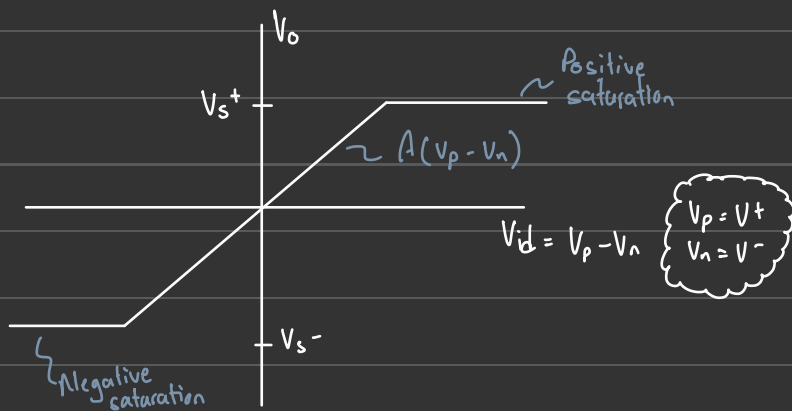Plotting output V vs input differential V



Ideal Op Amp

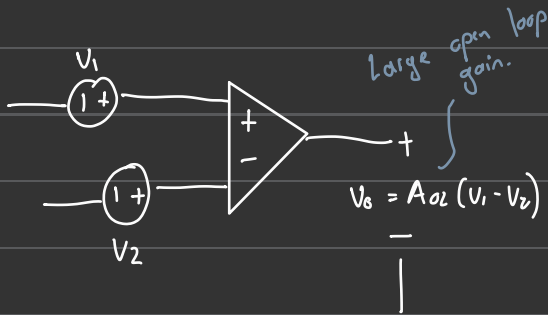

$$V_{icm} = \frac{1}{2} (V_1 + V_2)$$

Avg. between V_+ and V_-

$$V_{id} = V_+ - V_-$$
$$= V_1 - V_2$$

Assumptions

Infinite input impedance


Infinite differential gain

Zero common-mode gain

Zero output impedance

Infinite bandwidth

Negative feedback

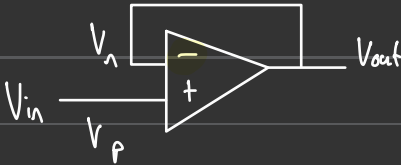

$$V_o = A(V_{in} - V_o)$$


$$V_{in} < V_o \Rightarrow V_o \downarrow$$

$$V_{in} > V_o \Rightarrow V_o \uparrow$$

V_o tends to V_{in}

$$\Rightarrow V_n = V_p$$

Positive feedback

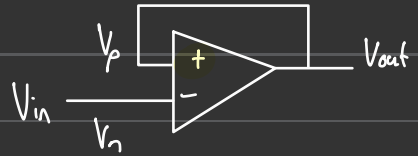

$$V_o = A(V_o - V_{in})$$

$$\bullet V_{in} < V_o \Rightarrow V_o \nearrow \text{Rail}$$

$$\bullet V_{in} > V_o \Rightarrow V_o \searrow \text{Rail}$$

Method

- 1) Confirm negative feedback
 ↳ Looking at feedback loop. $V_p = 0$ if connected directly to ground.
- 2) Assume $V_n = V_p$ and $i_n = i_p = 0$ A (bc. ∞ input impedance)
- 3) Use standard circuit analysis to determine values. ($A_v, R_i, R_{out}...$)
 ↳ KCL, KVL.... (usually KCL @ V_n)
- 4) Test that the op-amp is in between the linear region.


Inverting Amplifiers

From steps above:

$$\text{Gain: } A_v = \frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$

$$\text{Input } R: R_i = R_1$$

$$\text{Output } R: R_o = 0 \Omega$$

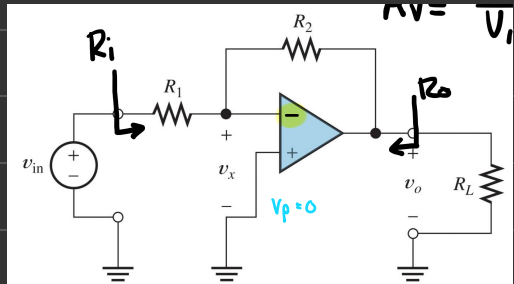


↳ V_{in} goes to \ominus side

Non-inverting Amplifiers

$$\text{Gain: } A_v = 1 + \frac{R_2}{R_1} \quad \left\{ \begin{array}{l} \text{not} \\ \text{always?} \end{array} \right.$$

$$R_i = \infty$$

$$R_o = 0 \Omega$$

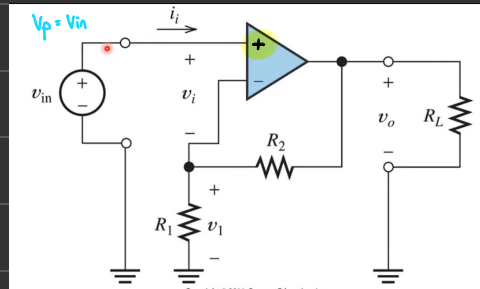

↳ V_{in} goes to \oplus side

Inverting summing Amp.


V_o is sum of V_A and V_B

Voltage follower / buffer


"protects equipment for surges"

$$V_o = V_{in}$$

$$R_{in} = \infty$$

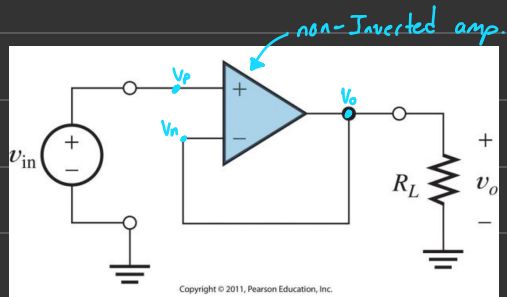

Designing a simple amplifier

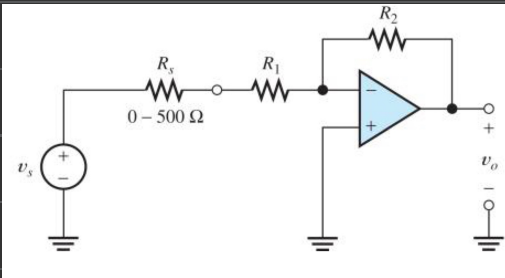

Gain \oplus \ominus
non-Inverting
Inverting

use $A_v = \frac{v_o}{v_{in}}$ to find R

Non-linear limitations: (cutoffs)


Recall $A_v = 1 + \frac{R_2}{R_1}$

↖ "around" for
real amps.

- Output swing: V_o will clip at the rail voltage.
This can be asymmetric if top and bottom rail voltages differ.

- Output current limits: Clipping occurs if the max output current limit is reached. ($I_o = \frac{V_o}{R}$)

- Slew-rate: $SR = \left| \frac{dV_o(t)}{dt} \right| = V_{om} 2\pi f_{FB} \text{ [V/s]}$

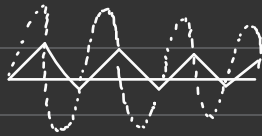

- full power BW: range of freq for which op-amp can produce an undistorted sinusoidal output with peak amplitude equal to the guaranteed maximum output.



$$f_{FB} = \frac{SR}{2\pi V_{om}} \rightarrow \text{guaranteed max output}$$

↪ so above this freq, we will hit slew rate




Differential op-amp

not Invert or non-invert.

To use this safely with instruments:

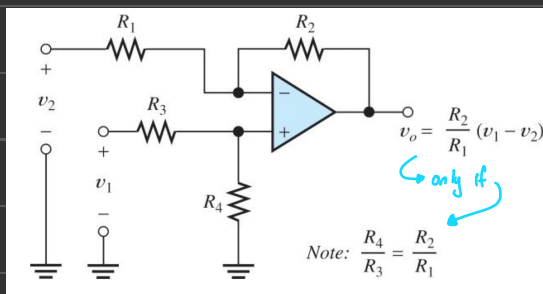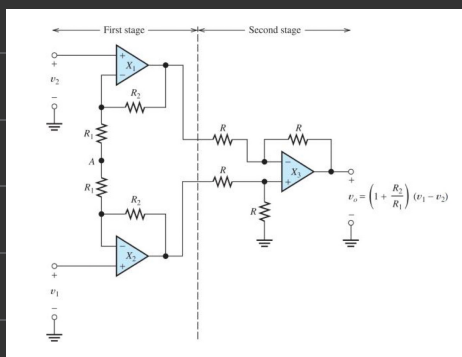

Integrators

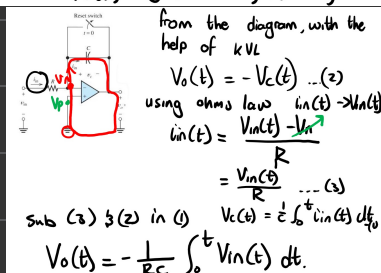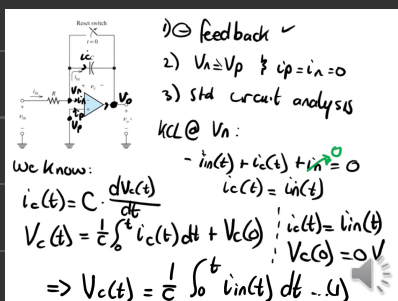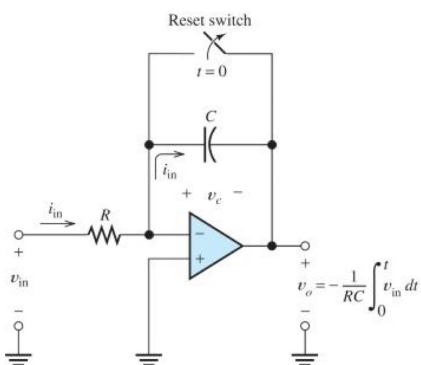

Differentiator

